

Power Electronics Technology

Exhibition & Conference

30 October 2002

Solving EMI for Low Wattage Universal Input Power Supplies

Authors

ON Semiconductor

Jim Spangler

Carl Walding

Dennis Jodlowski

Schaumburg, Illinois

CEC

Dave Pacholok

Sleepy Hollow, Illinois

Author Information

- Jim Spangler
 - jim.spangler@onsemi.com
 - 847-330-6963
 - Dennis Jodlowski
 - dennis.jodlowski@onsemi.com
 - 847-330-6957
 - Carl Walding
 - carl.walding@onsemi.com
 - 847-330-6965
 - ON Semiconductor
 - 1515 Woodfield Rd
 - Suite 745
 - Schaumburg, Illinois 60173
 - Dave Pacholok
 - davep@cecone.com
 - 847-428-5676
 - 847-426-9217 fax
 - CEC
 - 1515 Higgins Rd
 - Sleepy Hollow, Ill 60118
 - www.cecone.com

Purpose of the paper

- Cookbook to help design universal input flyback switching power supplies.
- Help understand the various techniques used on their effects of reducing EMI.
- Help reduce the engineering cycle time and improve the time to market of products.
- Educational tool to help novice switching power supplies engineers solve a sometimes black magic item


Example: TV Set-Top Box

- Universal input (85-270 Vac 47-63 Hz).
- 2-wire AC input (no earth ground plug).
- Multiple outputs all referenced to a common ground.
- 20 Watts.
 - $V_{out} = 3.3, 5.0, 12.0,$ and (32 or 38 LNB)
 - Flyback topology used for tracking and cross regulation.
- 2 options: Fixed Frequency (NCP1000) and the Critical Conduction Mode (MC33364)

FCC limits

- FCC
 - Class B (Consumer Limits)
 - Part 15, sub-part J
- Spectrum Analyzer
 - HP 8562A peak detector
 - HP E7401A EMI Analyzer
- Line Impedance Stabilization Network (LISN)
 - EMCO #3810/2 (modified 0.1 uF for FCC)
 - Discrete Dual per FCC specification (Dave Pacholok)

Line Conducted Limits

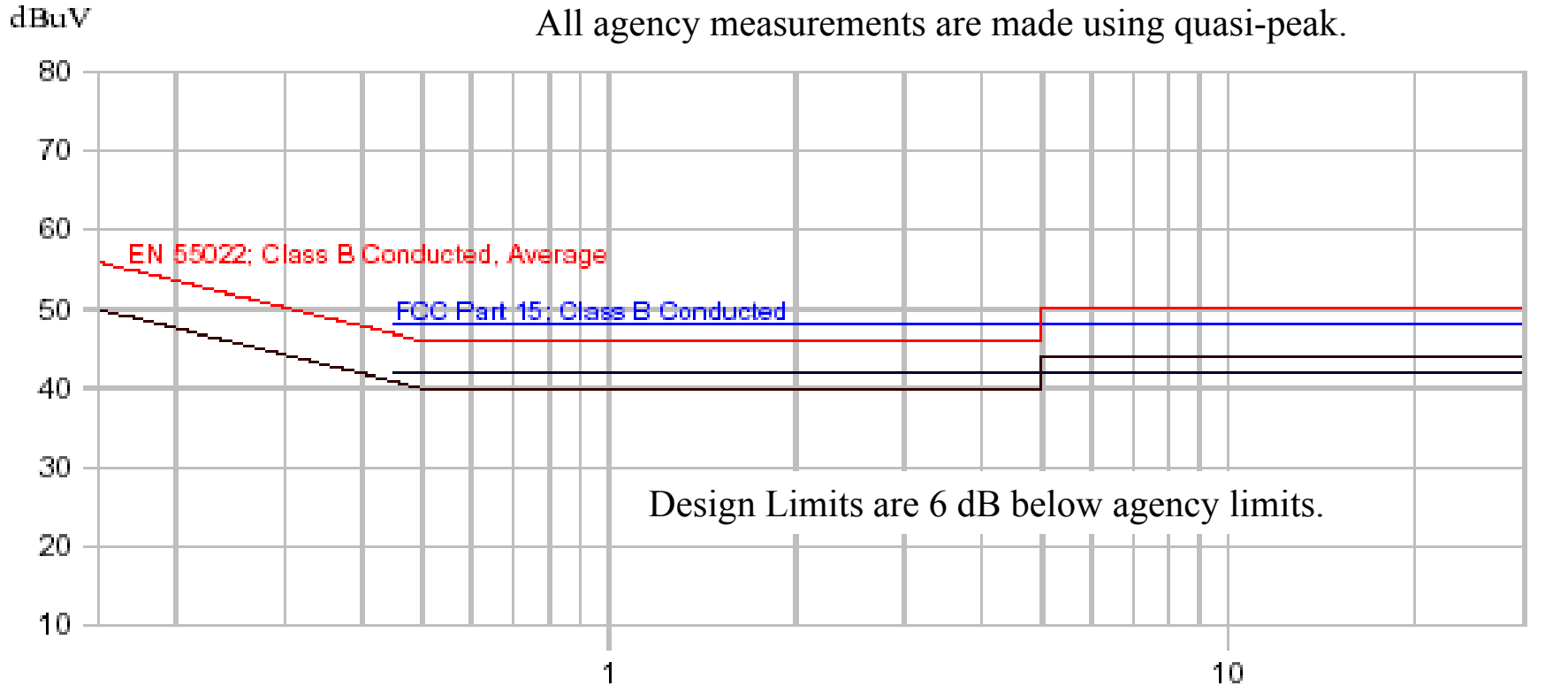


10/18/02 12:10:44 PM

(Start = 0.15, Stop = 30.00) MHz

Frequency MHz	Peak dBuV	QP dBuV	Avg dBuV	Trace Name	Comment
------------------	--------------	------------	-------------	------------	---------

FCC style LISN

(Line Impedance Stabilization Network)

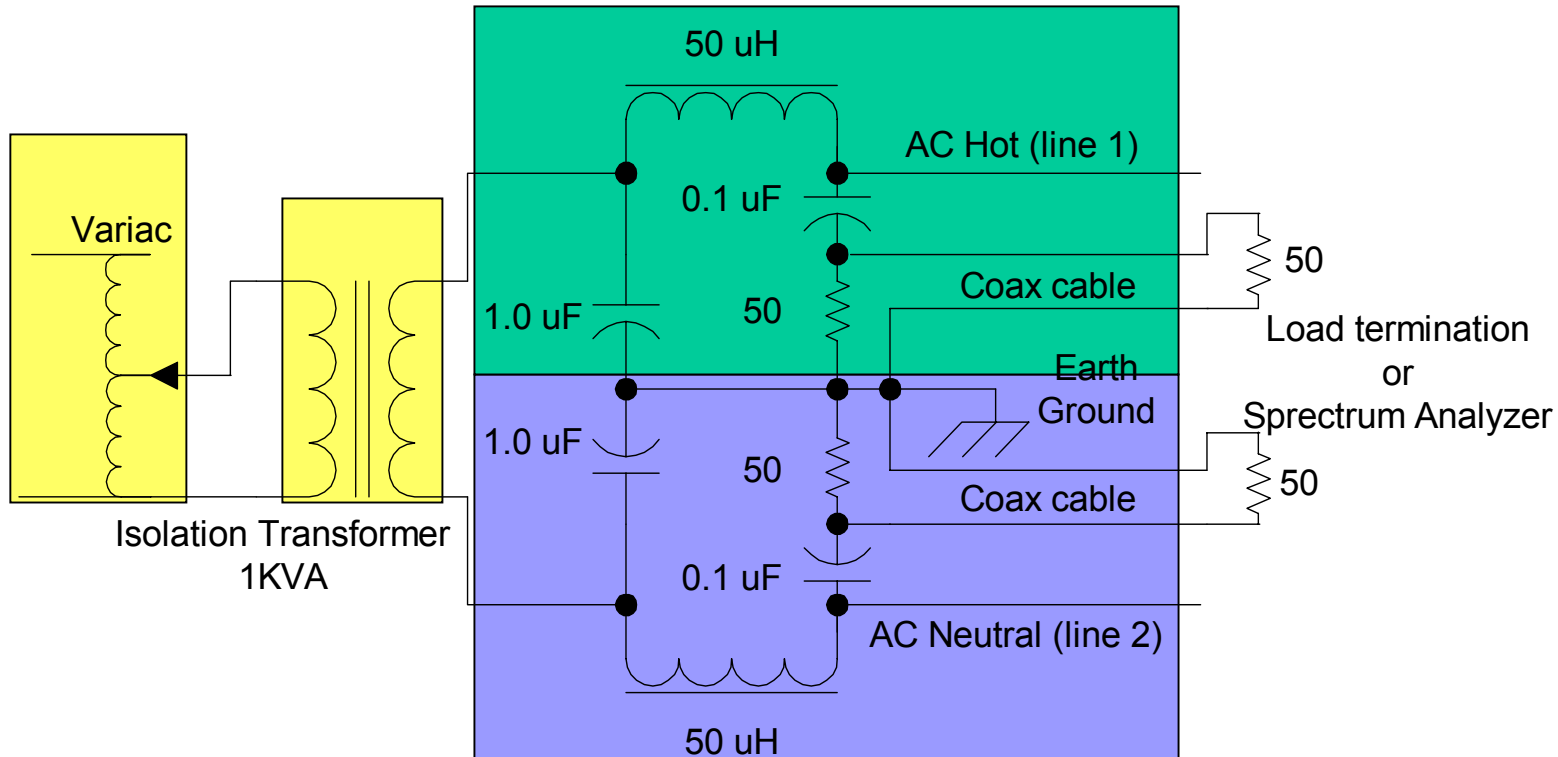


CISPR 0.47 uF Coupling Capacitor

Circuit Tools Available for Engineers


- Hot-Cold Ground Capacitor (Y-Capacitor)
- Common-Mode Choke
- Line-Line Capacitor (X-Capacitor)
- Transformer Snubber (DRC)
- Ferrite Beads (EMI suppression type)
- Switch RC Snubbber
- Output Diode Snubber (RC)
- Schottky Rectifier vs Ultra-Fast Rectifier

EMI Circuit Parts

20W Reference Design Using NCP1001

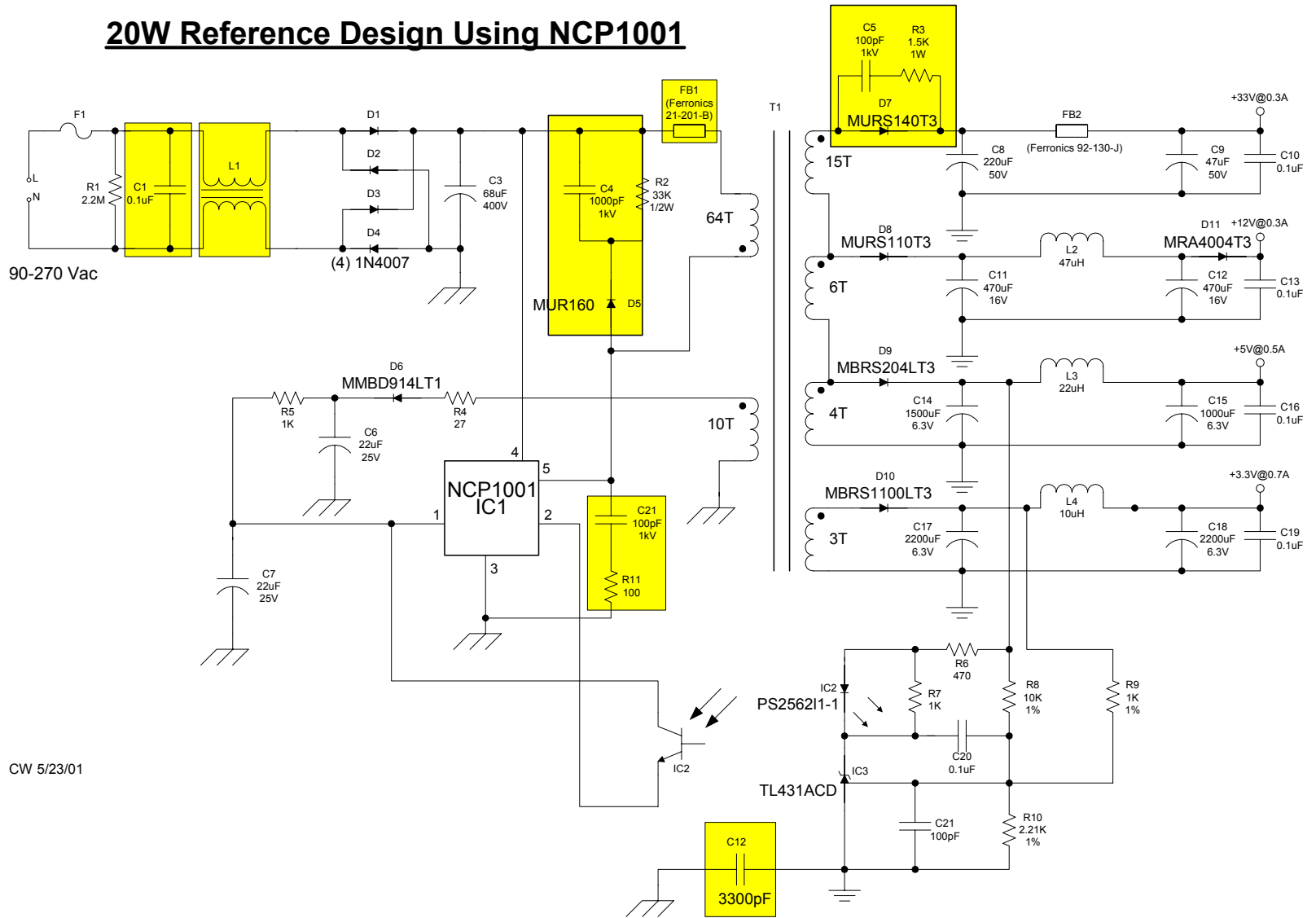

NCP1001 with no filtering

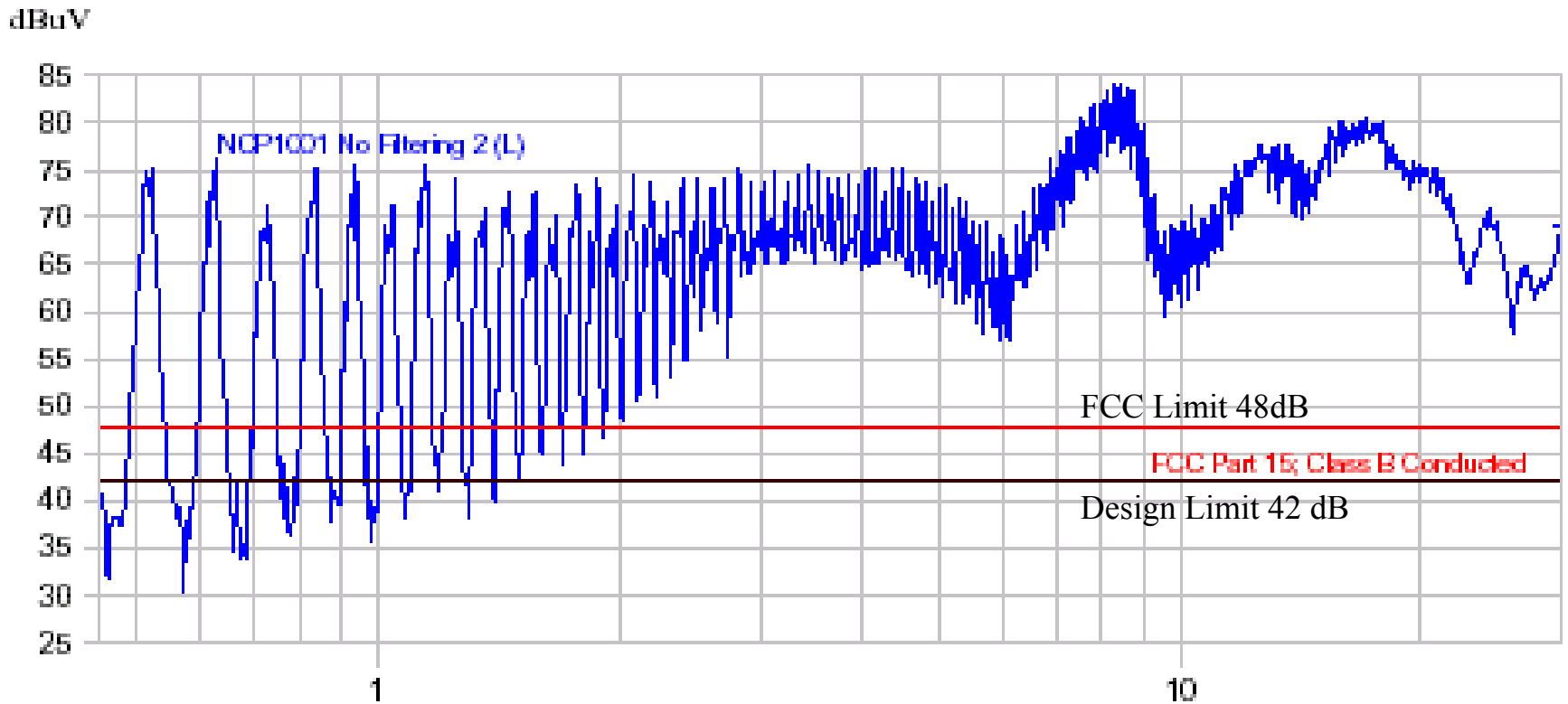

7/18/02 3:00:04 PM


(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta Pk-Limit dB	QP dBuV	Delta QP-Limit dB	Avg dBuV	Trace Name	Comment
------------------	--------------	----------------------	------------	----------------------	-------------	------------	---------

FCC indicates using highest Line or Neutral, only Line is shown here.

Hot to Cold Ground Cap. Schematic

20W Reference Design Using NCP1001

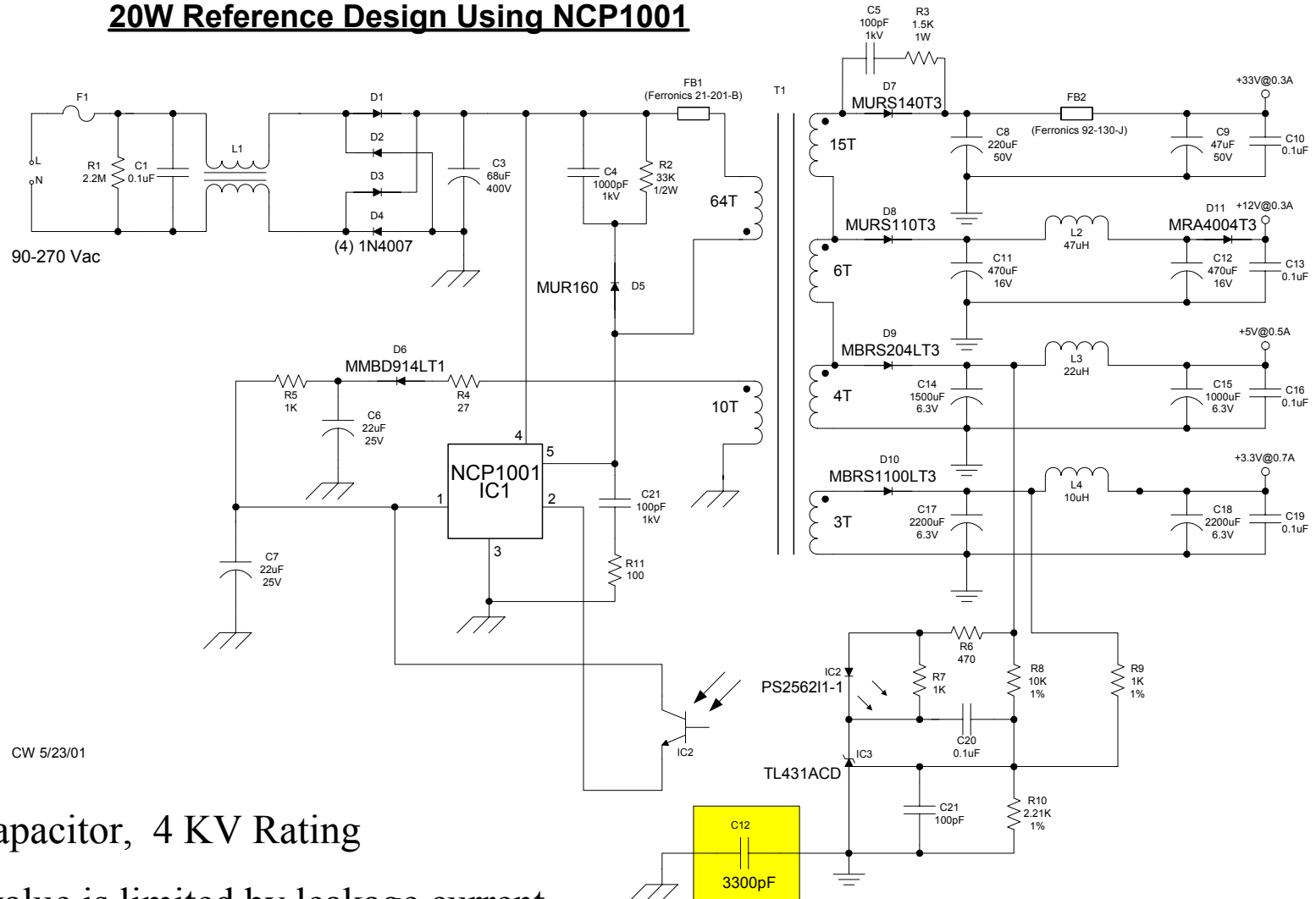


CW 5/23/01

“Y” Capacitor, 4 KV Rating

Max. value is limited by leakage current.



NCP1001 Hot-Cold Ground Cap (3300pF 4KV)

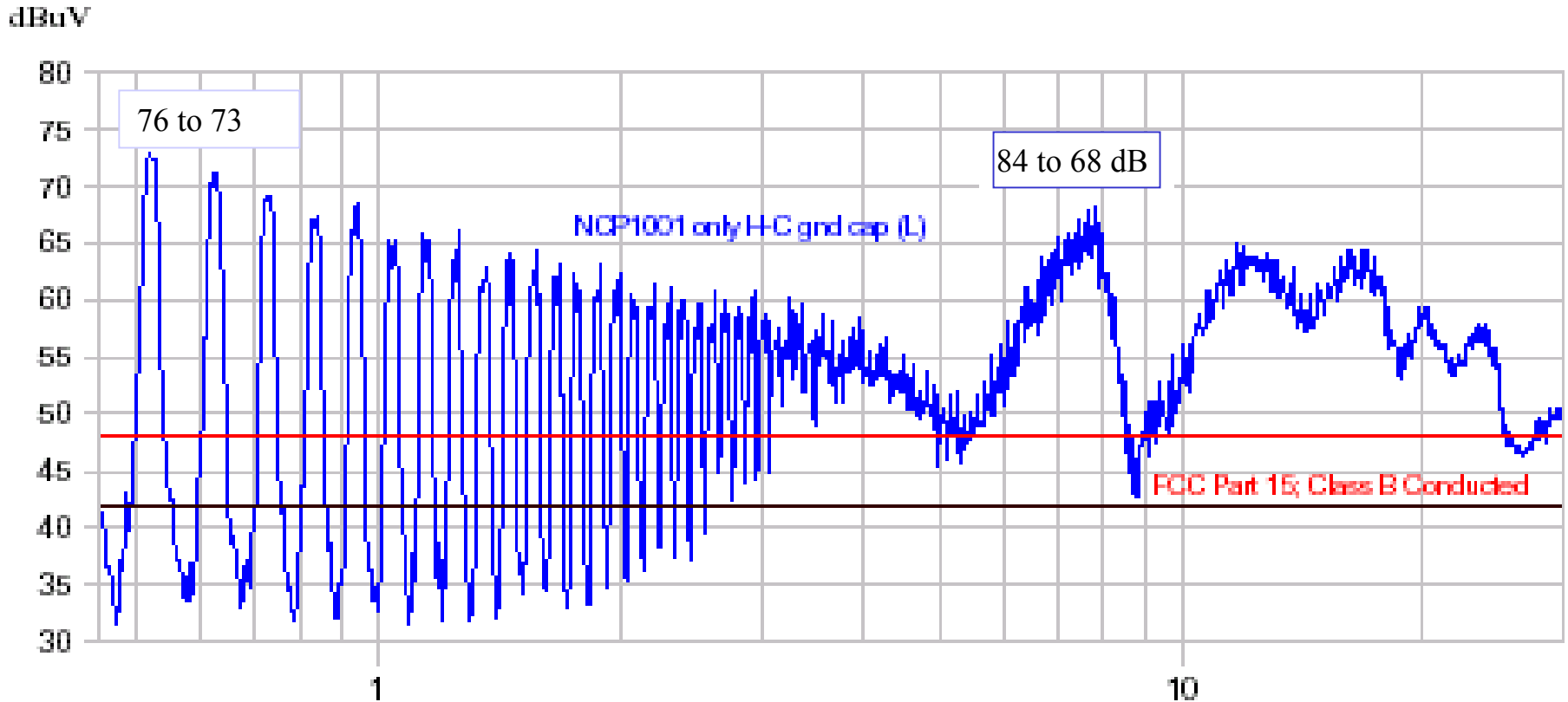

7/18/02 2:34:58 PM


(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta dB	Pk-Limit	QP dBuV	Delta dB	QP-Limit	Avg dBuV	Trace Name	Comment
------------------	--------------	-------------	----------	------------	-------------	----------	-------------	------------	---------



Common Mode Choke Schematic

20W Reference Design Using NCP1001

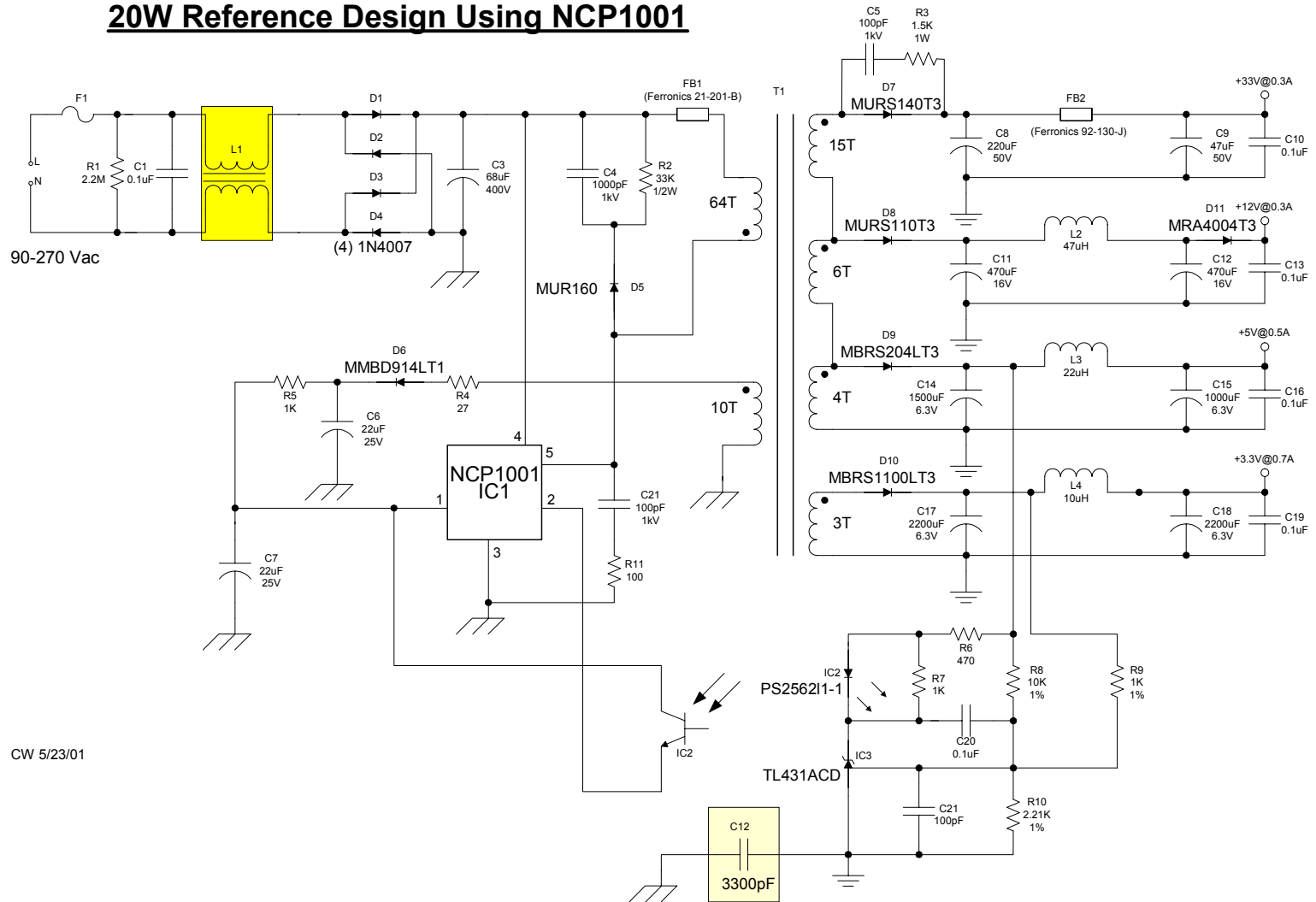

CW 5/23/01




Common Mode Choke

- Line Inductance Leg 39.4 mH
- Neutral Inductance Leg 39.4 mH
- Resistance per Leg 1.3 ohms
- Mutual Inductance 39.35 mH
- Coupling Coefficient 0.9975
- Capacitance between Sections 3.0 pF


Common Mode Choke Impedance Plot

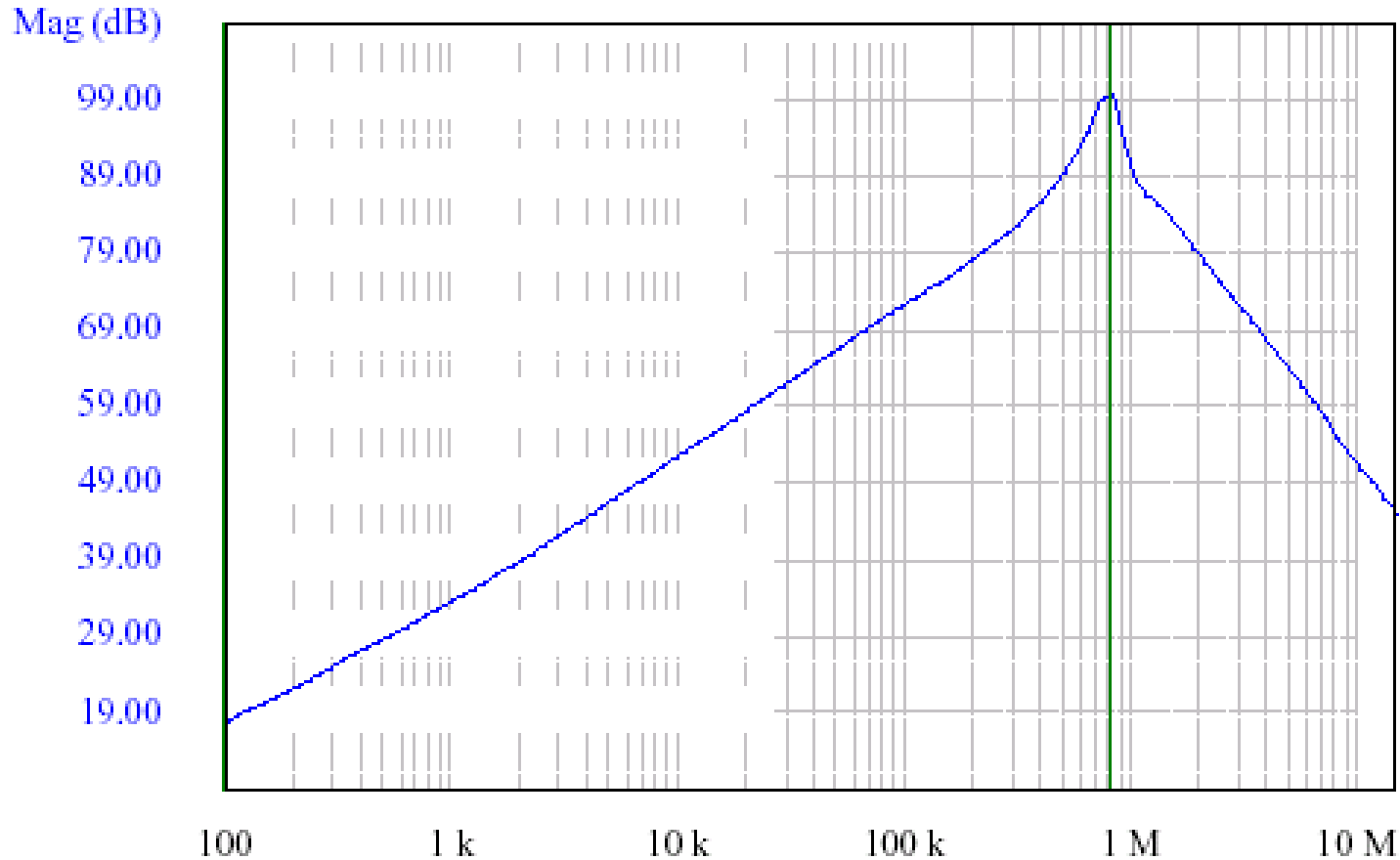Impedance (dBohms) - Delta LFZ20H03 Line Choke; 4 Bays; L=38mH, DCR=1.4ohms



AP102B Frequency Response Analyzer

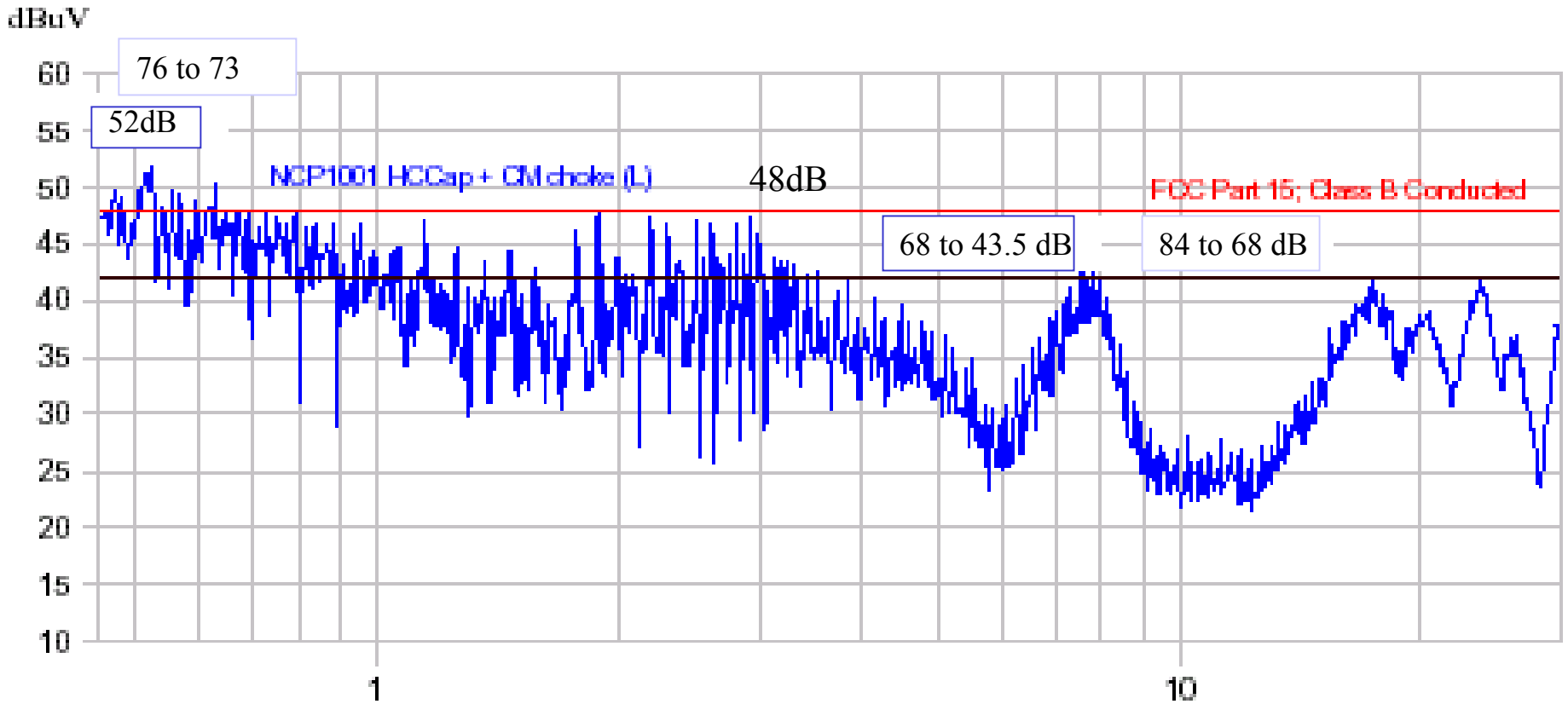Common Mode Choke with Hot-Cold Ground Capacitor



7/18/02 3:14:51 PM


(Start = 0.45, Stop = 30.00) MHz

Frequency MHz	Peak dBuV	Delta dB	Pk-Limit	QP dBuV	Delta dB	QP-Limit	Avg dBuV	Trace Name	Comment
------------------	--------------	-------------	----------	------------	-------------	----------	-------------	------------	---------



Line-Line Capacitor Schematic


20W Reference Design Using NCP1001

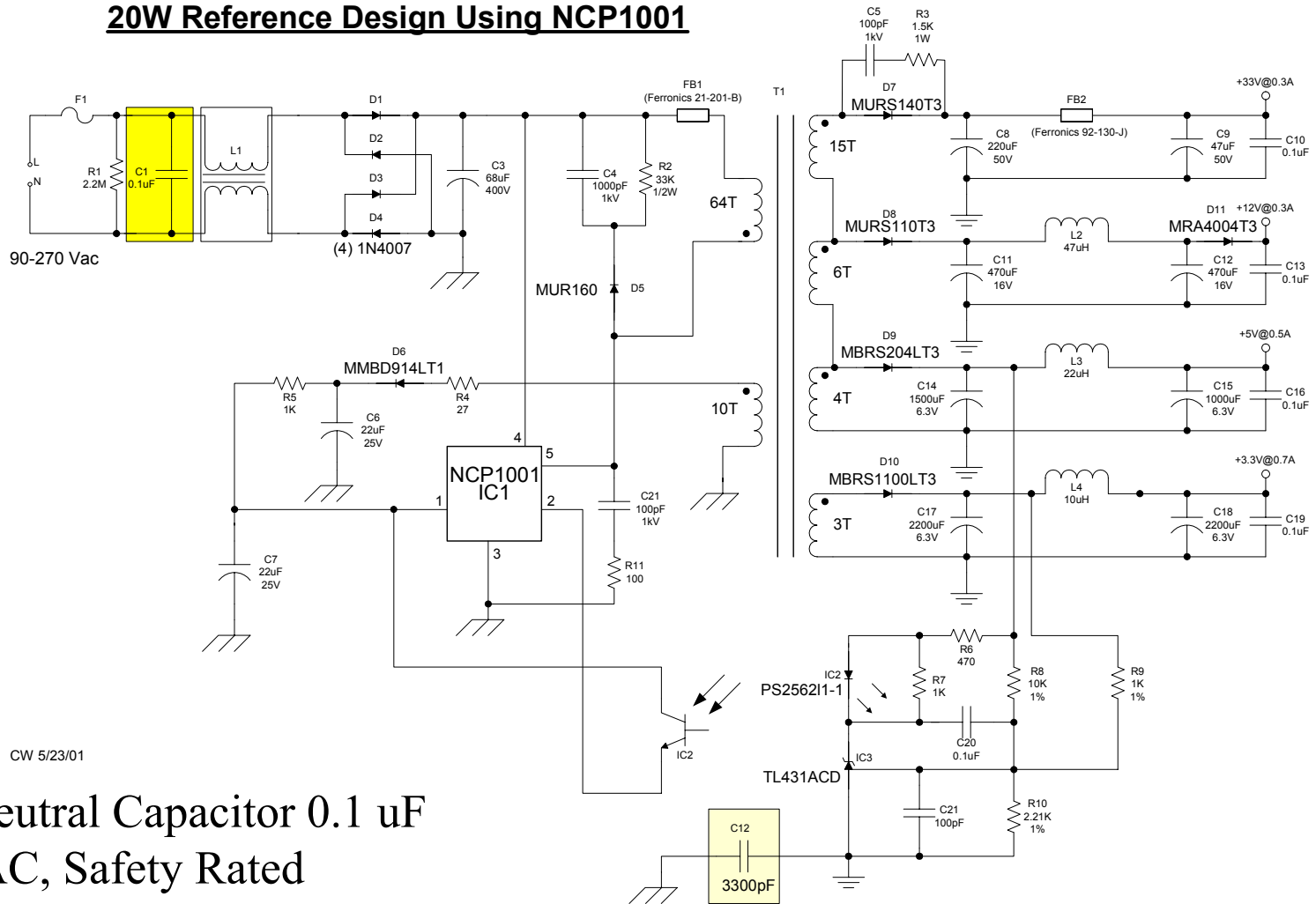

CW 5/23/01

Line-Neutral Capacitor 0.1 uF
250 VAC, Safety Rated

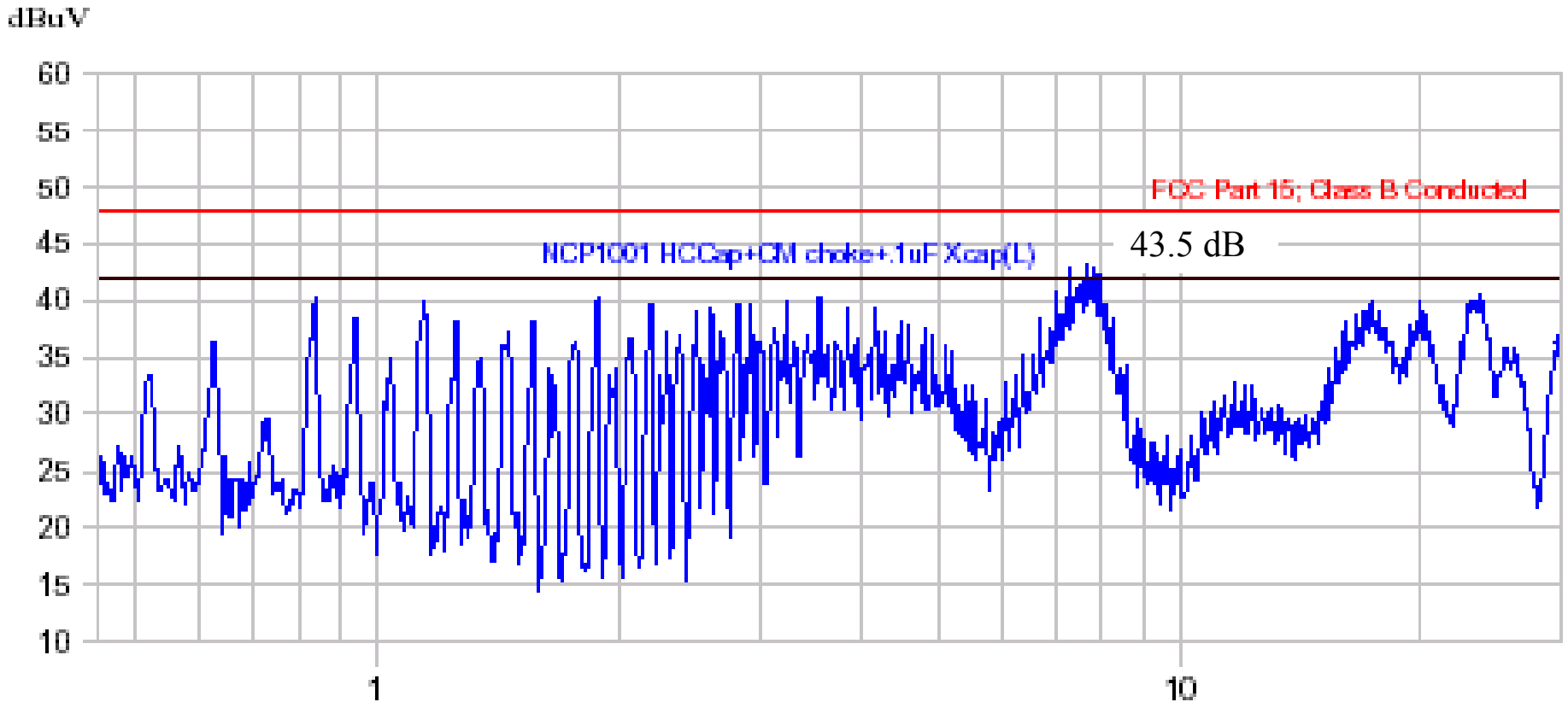Common Mode Choke with X Capacitor and H-Cap



7/18/02 3:26:00 PM

(Start = 0.45, Stop = 30.00) MHz


Frequency MHz	Peak dBuV	Delta Pk-Limit dB	QP dBuV	Delta QP-Limit dB	Avg dBuV	Trace Name	Comment
------------------	--------------	----------------------	------------	----------------------	-------------	------------	---------



Met the FCC Class B limit

- Just above the 42 dB spec. design limit.
 - Quasi peak vs Peak detect can add up to 2 dB of additional margin.
- Below the 48 dB FCC limits (Quasi Peak).
- 2-Wire system with NO Ground Plane
- Easily meets the Class A limits.
- What is the ground noise floor limit?

Ground Floor (log scale)

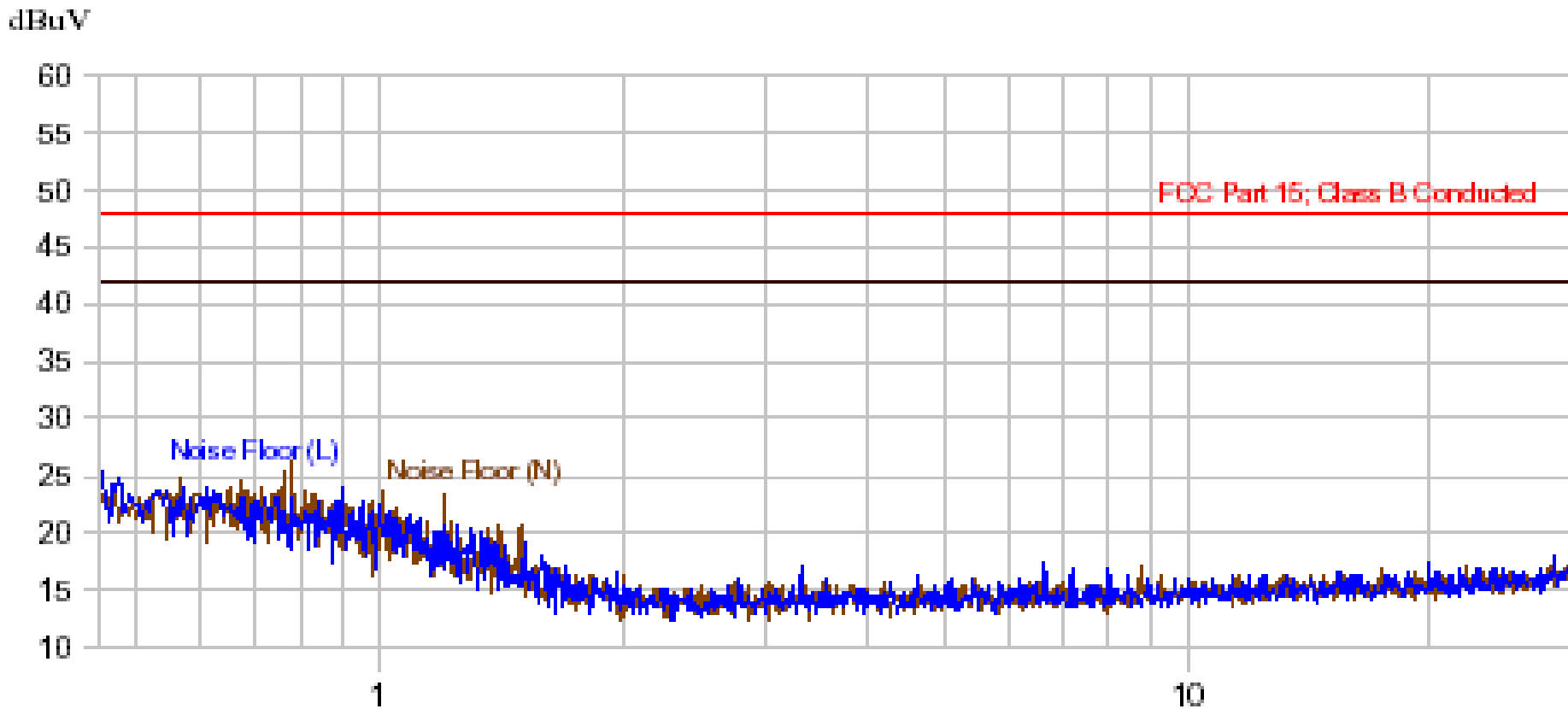


7/19/02 5:37:33 PM

(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta dB	Pk-Limit	QP dBuV	Delta dB	QP-Limit	Avg dBuV	Trace Name	Comment
------------------	--------------	-------------	----------	------------	-------------	----------	-------------	------------	---------



Ground Floor (Linear scale)

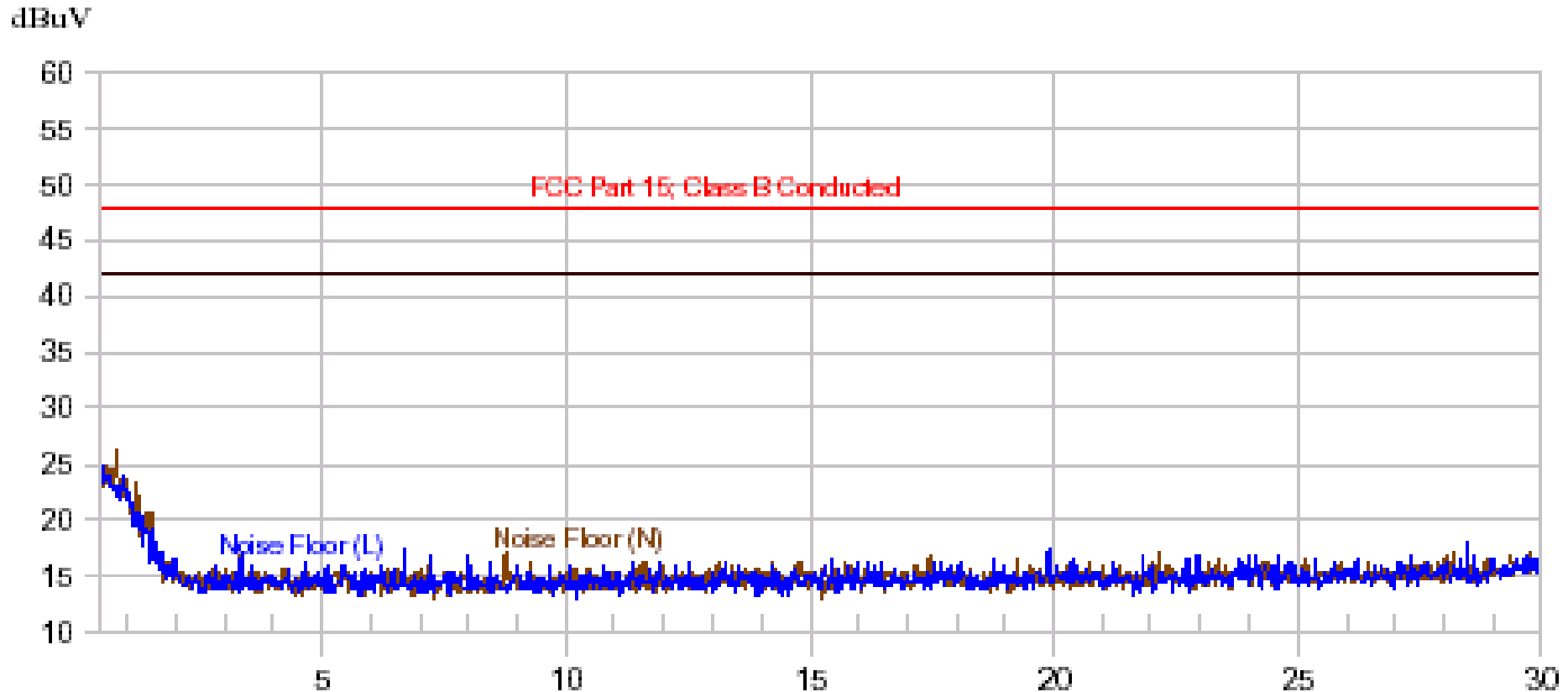


7/19/02 5:37:33 PM

(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta dB	Pk-Limit	QP dBuV	Delta dB	QP-Limit	Avg dBuV	Trace Name	Comment
------------------	--------------	-------------	----------	------------	-------------	----------	-------------	------------	---------



Additional Reductions

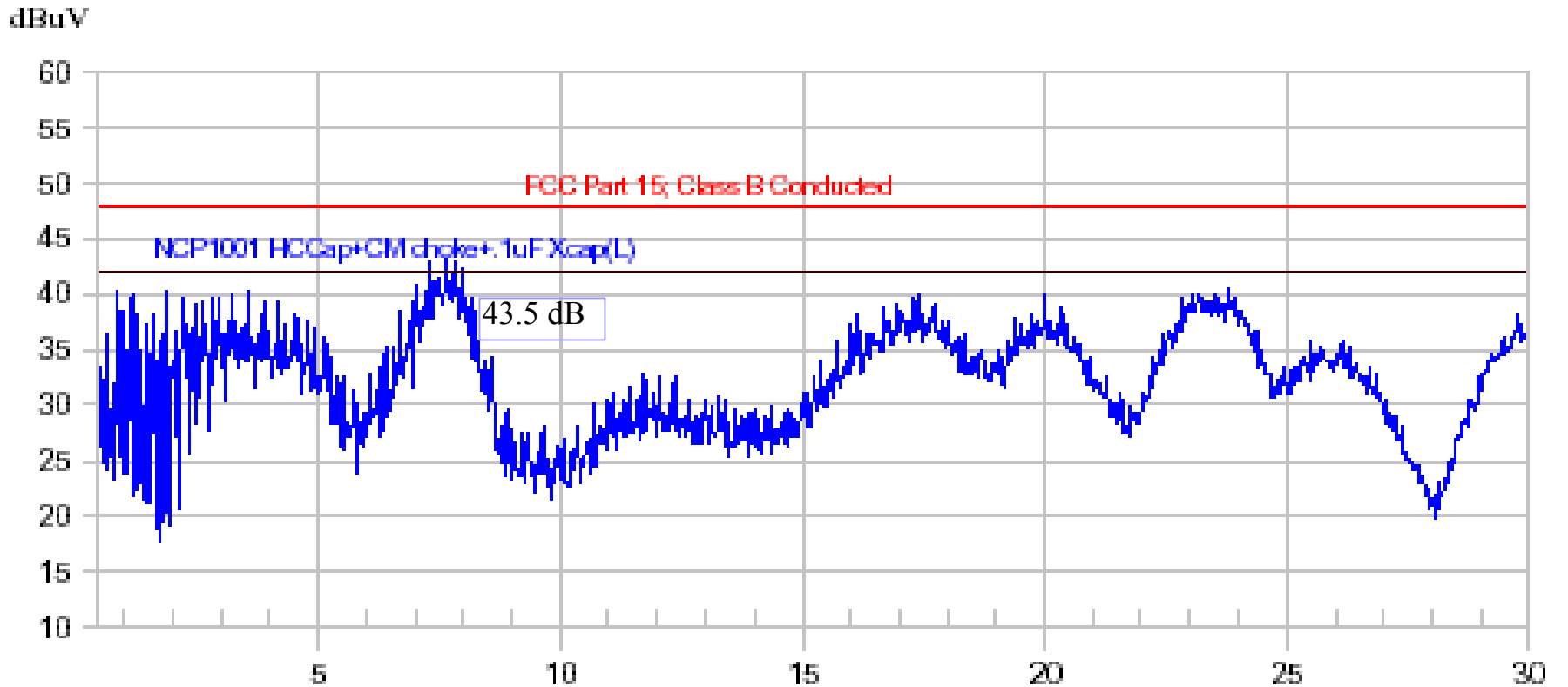

7/18/02 3:26:00 PM


(Start = 0.45, Stop = 30.00) MHz

Frequency MHz	Peak dBuV	Delta dB	Pk-Limit	QP dBuV	Delta dB	QP-Limit	Avg dBuV	Trace Name	Comment
------------------	--------------	-------------	----------	------------	-------------	----------	-------------	------------	---------




Switch Voltage and Current

20W Reference Design Using NCP1001

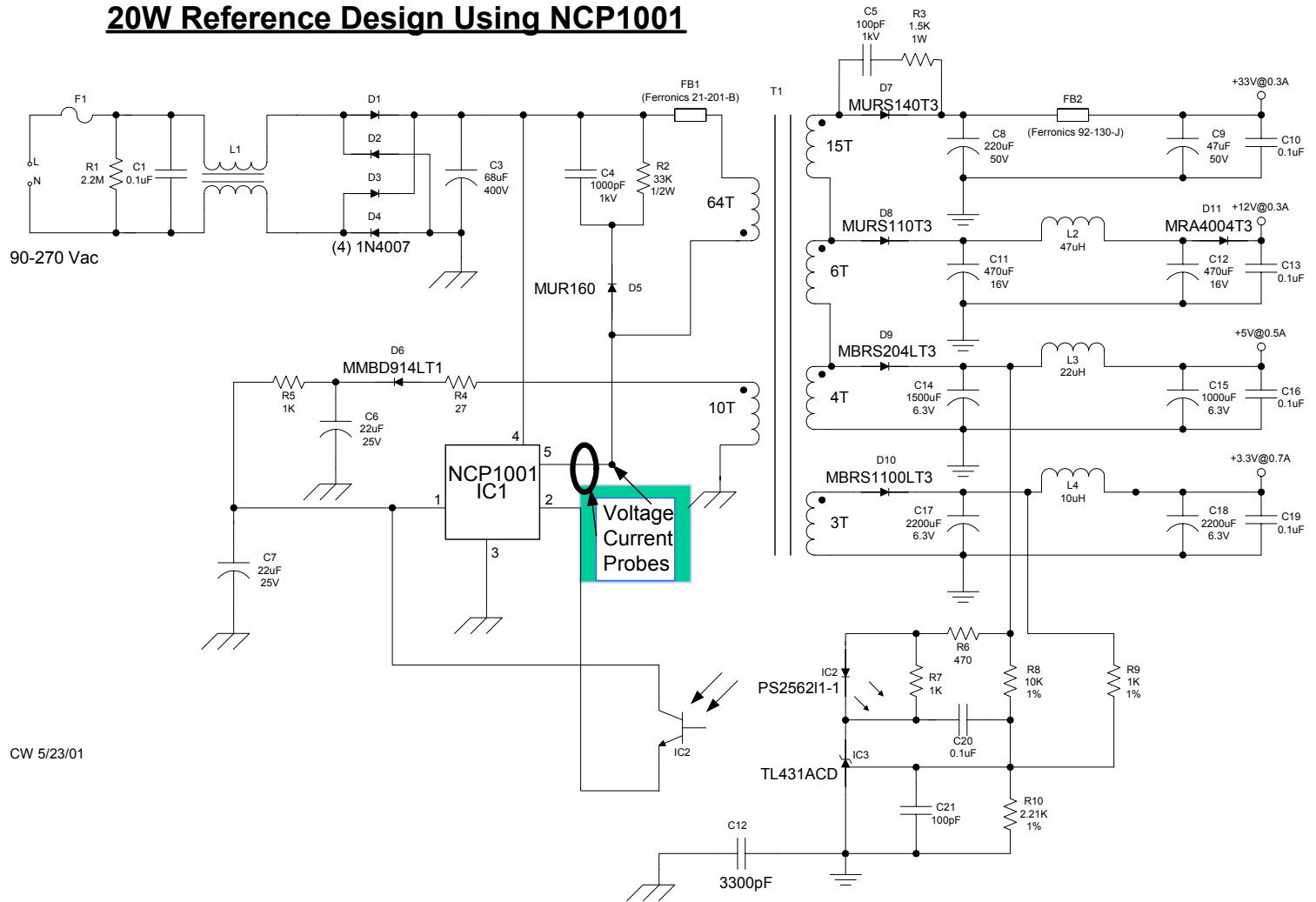


Transformer EMI Ringing

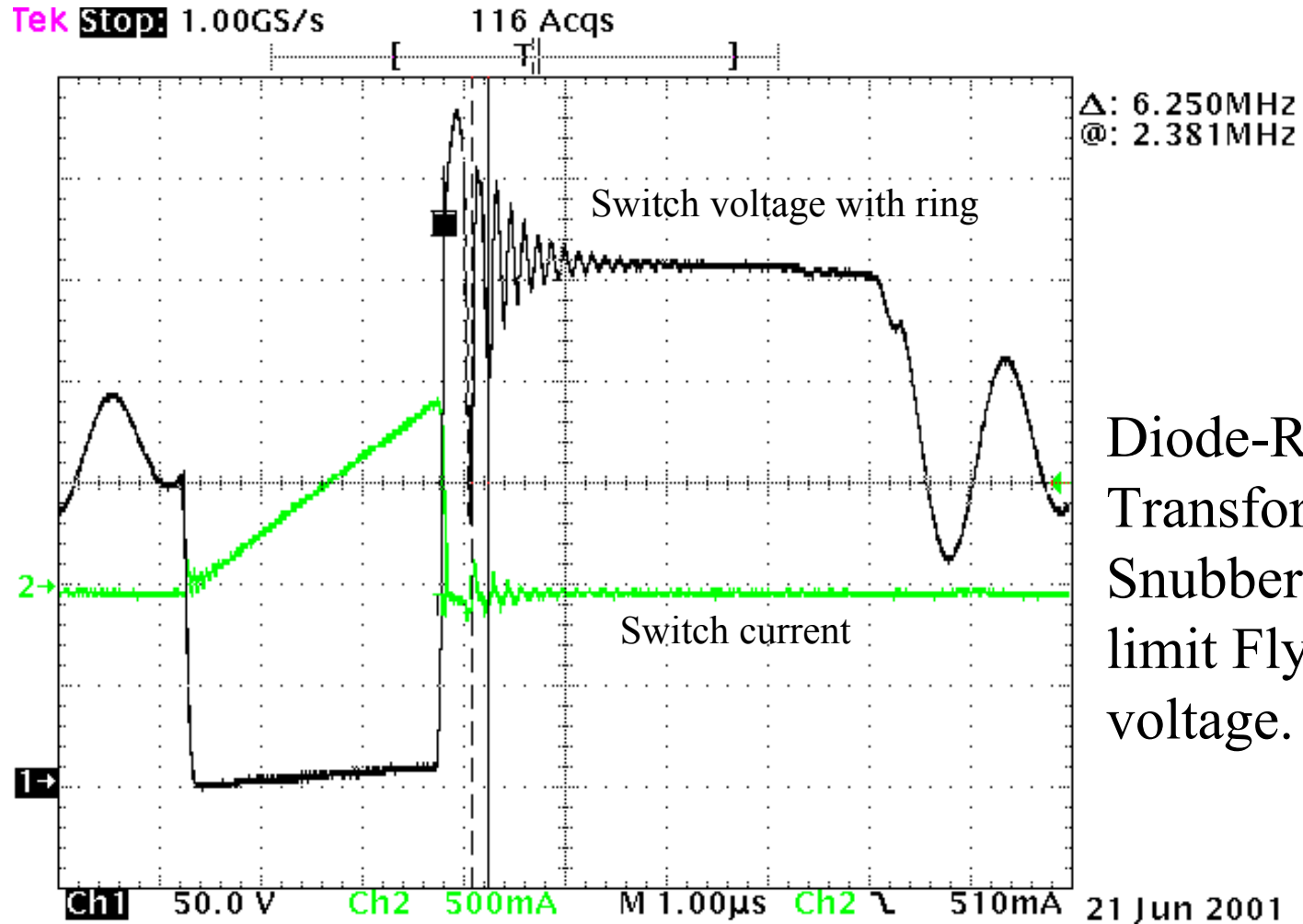

Diode-RC
Transformer
Snubber to
limit Flyback
voltage.

Ferrite Bead

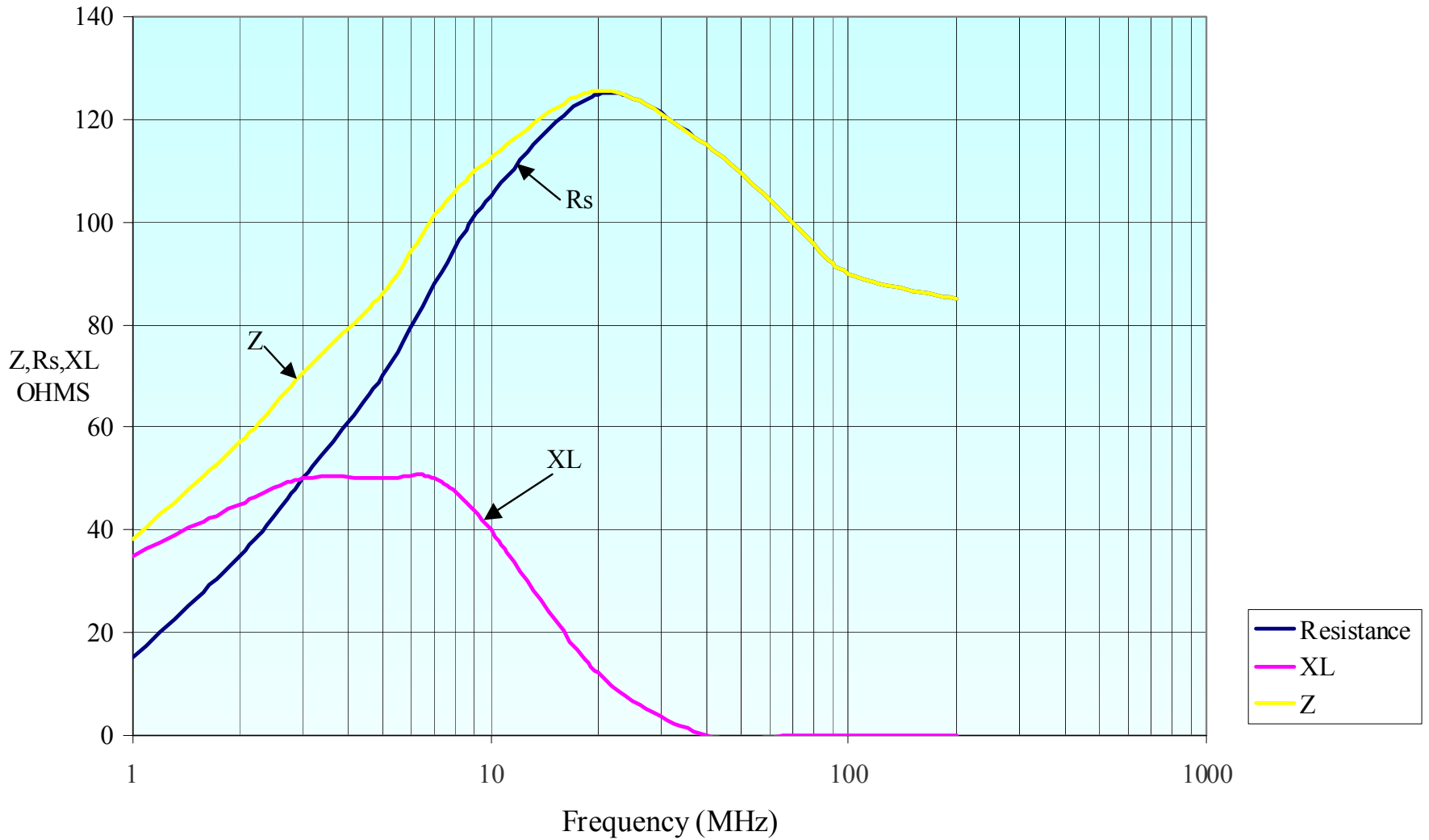
Fair-Rite Bead Characteristics
2773007112




Ferrite Bead 120 Vac

Tek Stop: 500MS/s


8 Acqs

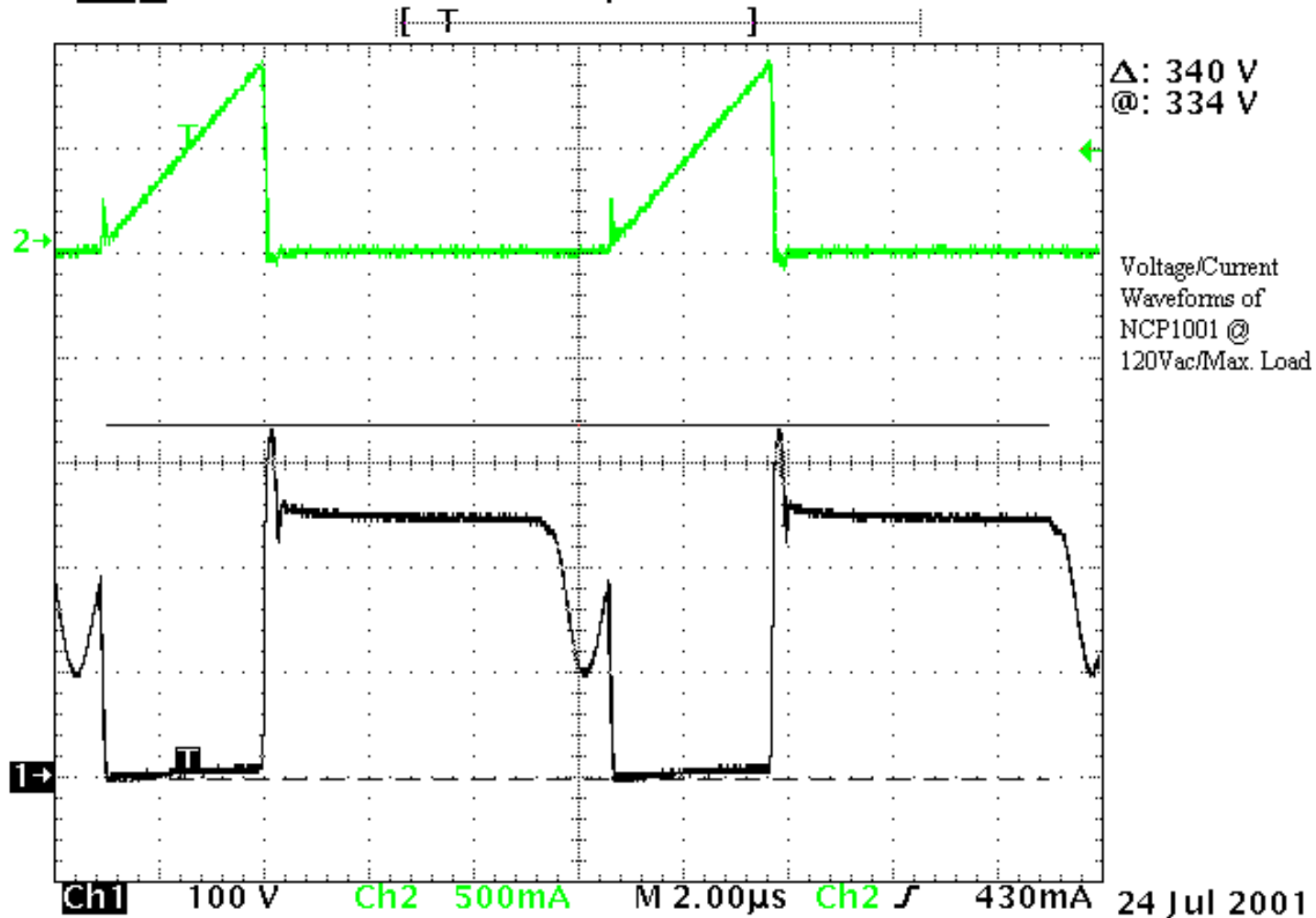


Ferrite Bead 220 Vac

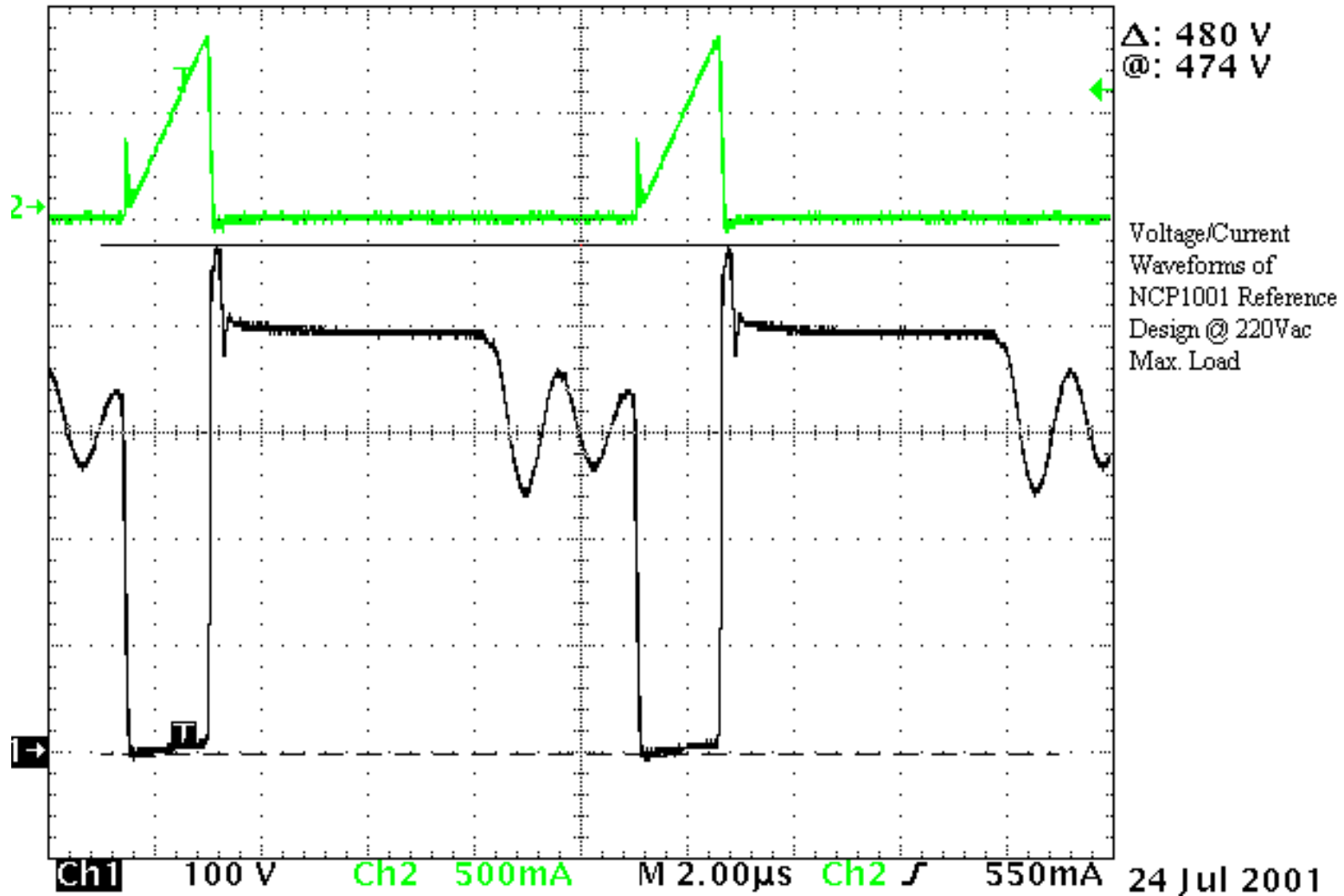

Reverse Recovery Diode (t_{rr} issues)

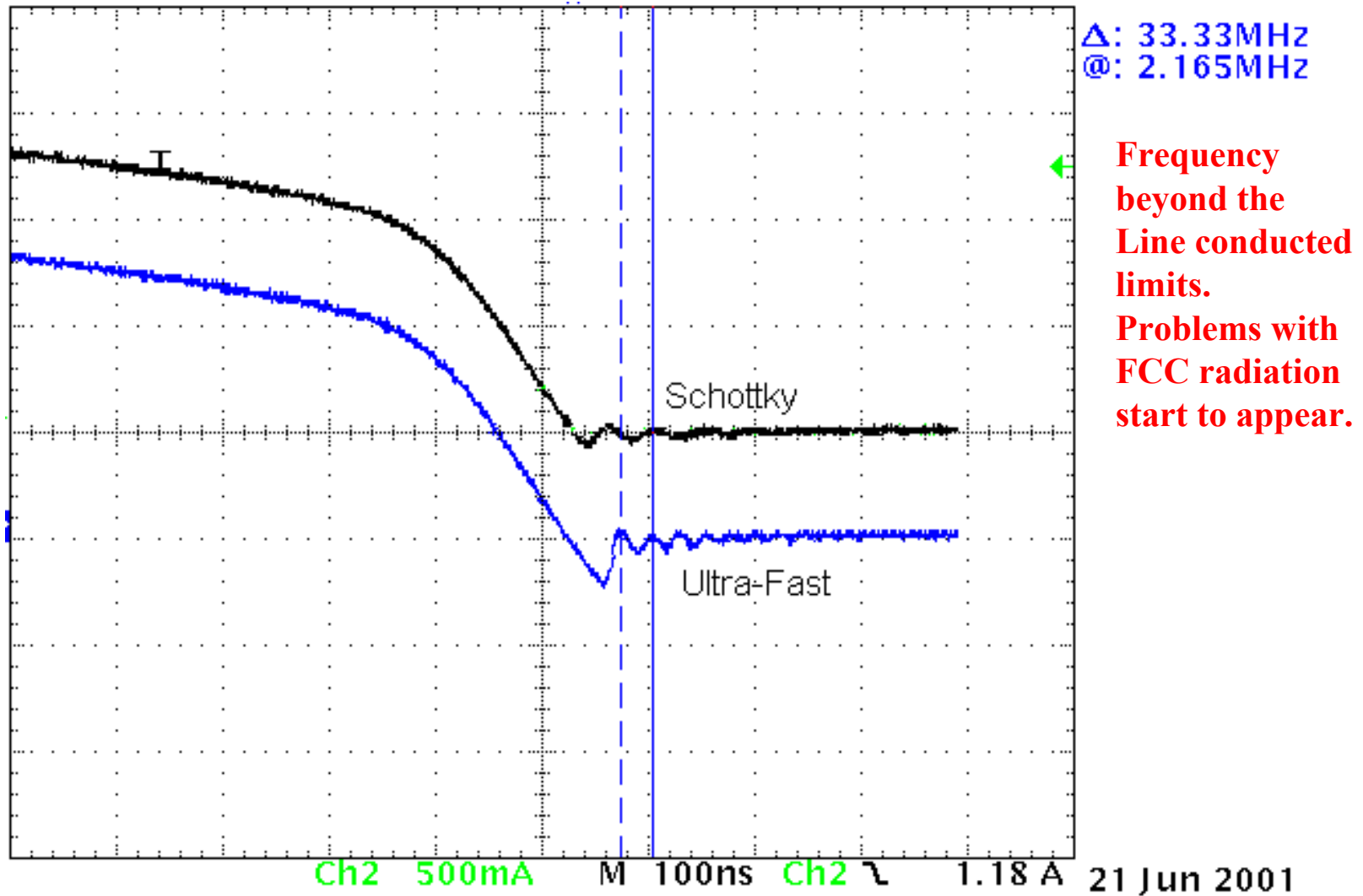

Ferrite Bead

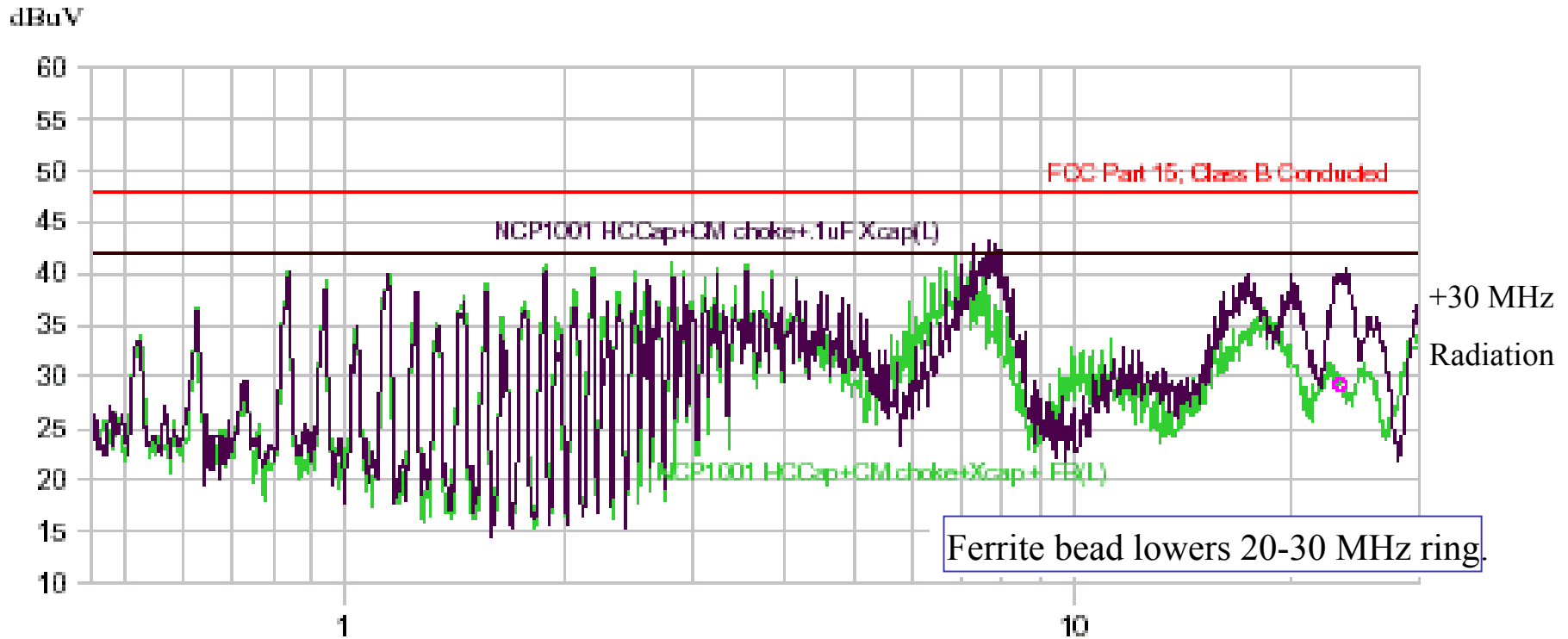

7/18/02 3:37:42 PM


(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta Pk-Limit dB	QP dBuV	Delta QP-Limit dB	Avg dBuV	Trace Name	Comment
23.218	29.2	-18.8				NCP1001 HCCap+CM choke+Xcap + FB(L)	



Ground Plane added beneath PC Board

20W Reference Design Using NCP1001

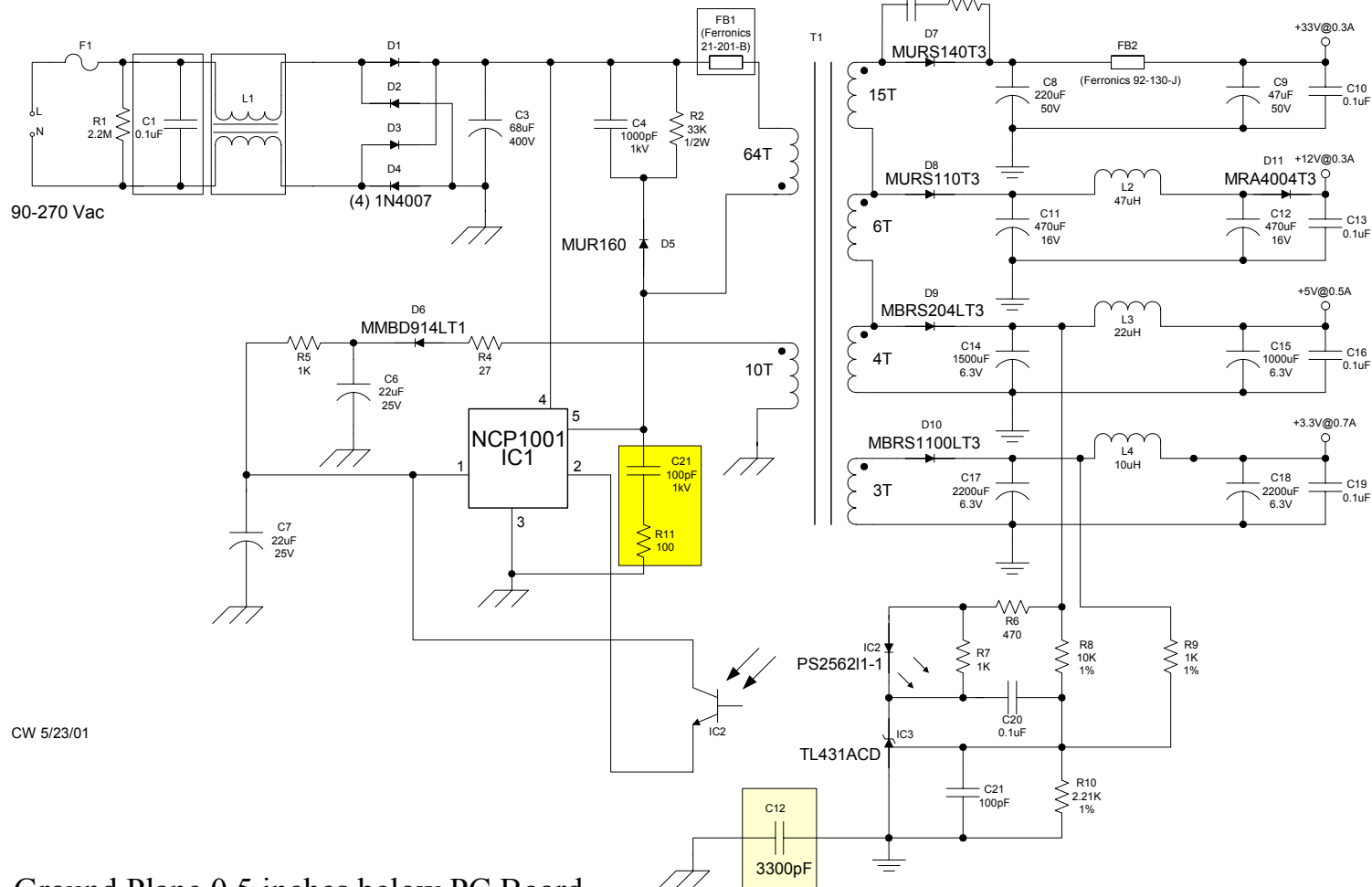


CW 5/23/01

Ground Plane 0.5 inches below PC Board

Ground Plane

Switch Snubber

100 pF-100 ohm

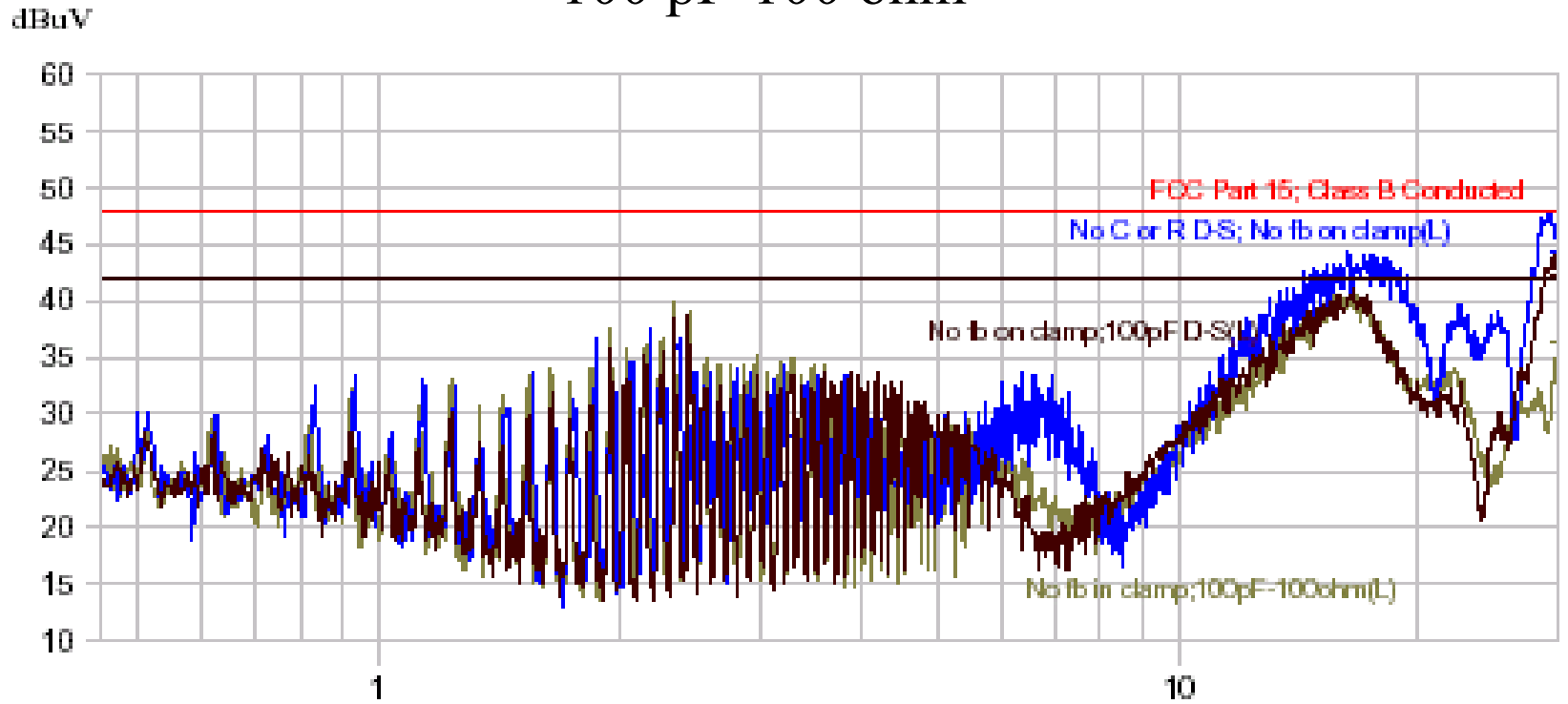


7/19/02 9:48:46 AM

(Start = 0.45, Step = 30.00) MHz

Frequency MHz	Peak dBuV	Delta Pk-Limit dB	QP dBuV	Delta QP-Limit dB	Avg dBuV	Trace Name	Comment
------------------	--------------	----------------------	------------	----------------------	-------------	------------	---------



Ground Plane added

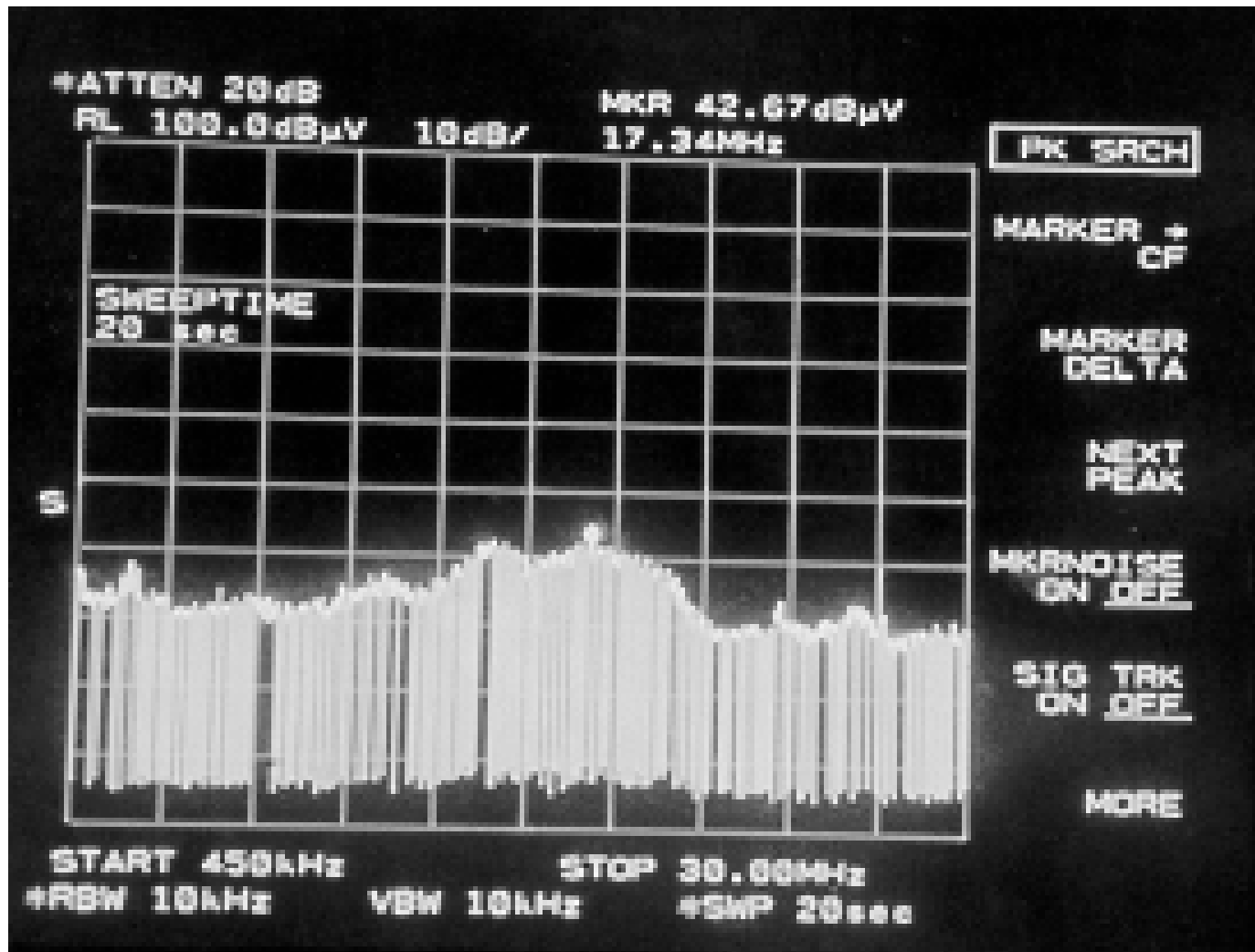

Other Sources of Information

- Ott, Henry, Noise Reduction Techniques in Electronic Systems, 1988 John Wiley
- Mills, Jeffrey, Electro-Magnetic Interference Reduction in Electronic Systems, 1993 Prentice Hall
- Ott, Henry, ‘Understanding and Controlling Common-Mode Emissions In High-Power Electronics’, Professional Education Seminars IEEE, APEC Mar. 2002
- Schutten, Michael, ‘EMI: Theory, Issues, and Solutions’, Professional Education Seminars IEEE, APEC Mar. 2002
- Class Notes ECE-522, Electro-Magnetic Compatibility, Dr. Jeff Mills, Illinois Institute of Technology.
- Dr. Ridley, Power 4-5-6. Ver 8.0, Snubber design

Thank You,
Comments,
? Questions ?

For copy of the presentation in pdf format, please
give Carl, Dennis, or my self a business card.